

GATE-EC-51


EE23BTECH11059- Tejas Mehtre*

Consider an FM broadcast that employs the pre-emphasis filter with frequency response

$$H_{pe}(\omega) = 1 + \frac{j\omega}{\omega_0},$$

where $\omega_0 = 10^4$ rad/sec.

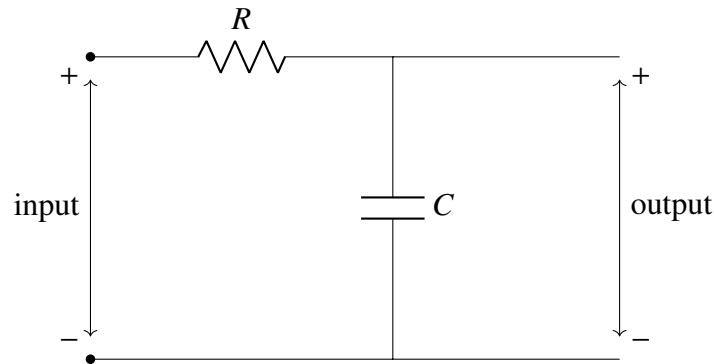For the network shown in the figure to act as a corresponding de-emphasis filter, the appropriate pair(s) of (R,C) values is/are _____



- A. $R = 1k\Omega$, $C = 0.1\mu F$
- B. $R = 2k\Omega$, $C = 1\mu F$
- C. $R = 1k\Omega$, $C = 2\mu F$
- D. $R = 2k\Omega$, $C = 0.5\mu F$

Solution:

Variable	Description	Value
H_{pre}	Frequency response of pre-emphasis filter	$1 + j\frac{\omega}{\omega_0}$
ω_0	Fundamental Frequency	10^4 rad/sec

TABLE 0

INPUT PARAMETERS

Taking KVL around the loop,

$$-V_i(t) + i(t)R + V_0(t) = 0 \quad (1)$$

$$\mathcal{L}(f'(t)) = sF(s) - f(0) \quad (2)$$

$$i(t) = C \frac{dV_0(t)}{dt} \quad (3)$$

Using (2) and (3),

$$\mathcal{L}\left(-V_i(t) + RC\frac{dV_0(t)}{dt} + V_0(t)\right) = \mathcal{L}(0) \quad (4)$$

$$V_0(s)(1 + j\omega RC) = V_i(s) \quad (5)$$

$$H(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)} = \frac{1}{1 + j\omega RC} \quad (6)$$

The given RC circuit to act as de-emphasis filter

$$|H(j\omega)| = \frac{1}{|H_{pre}(\omega)|} \quad (7)$$

$$\frac{1}{\sqrt{1 + (\omega RC)^2}} = \frac{1}{\sqrt{1 + \left(\frac{\omega}{\omega_0}\right)^2}} \quad (8)$$

$$\omega_0 = \frac{1}{RC} \quad (9)$$

$$\omega_0 = 10^4 \text{ rad/sec} \quad (10)$$

Thus $\omega_0 = 10^4$ rad/sec only possible if we choose $R = 1k\Omega$ and $C = 0.1\mu F$ from options. Hence, the correct option is (B).

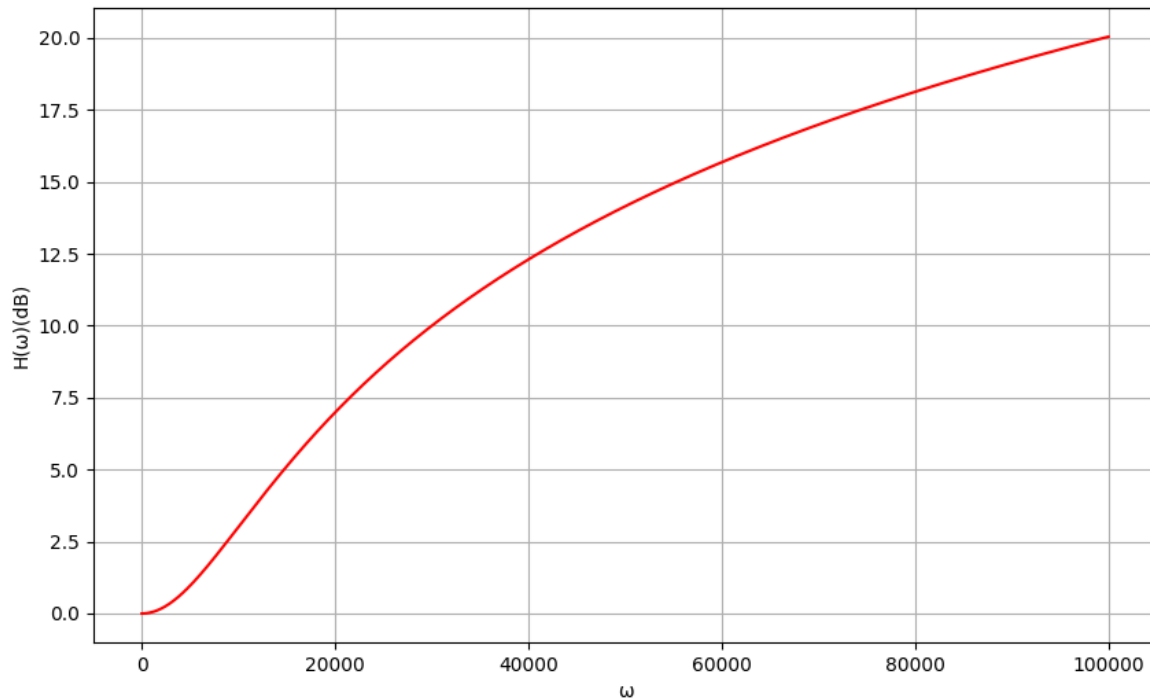


Fig. 0. Transient response of a pre-emphasis filter